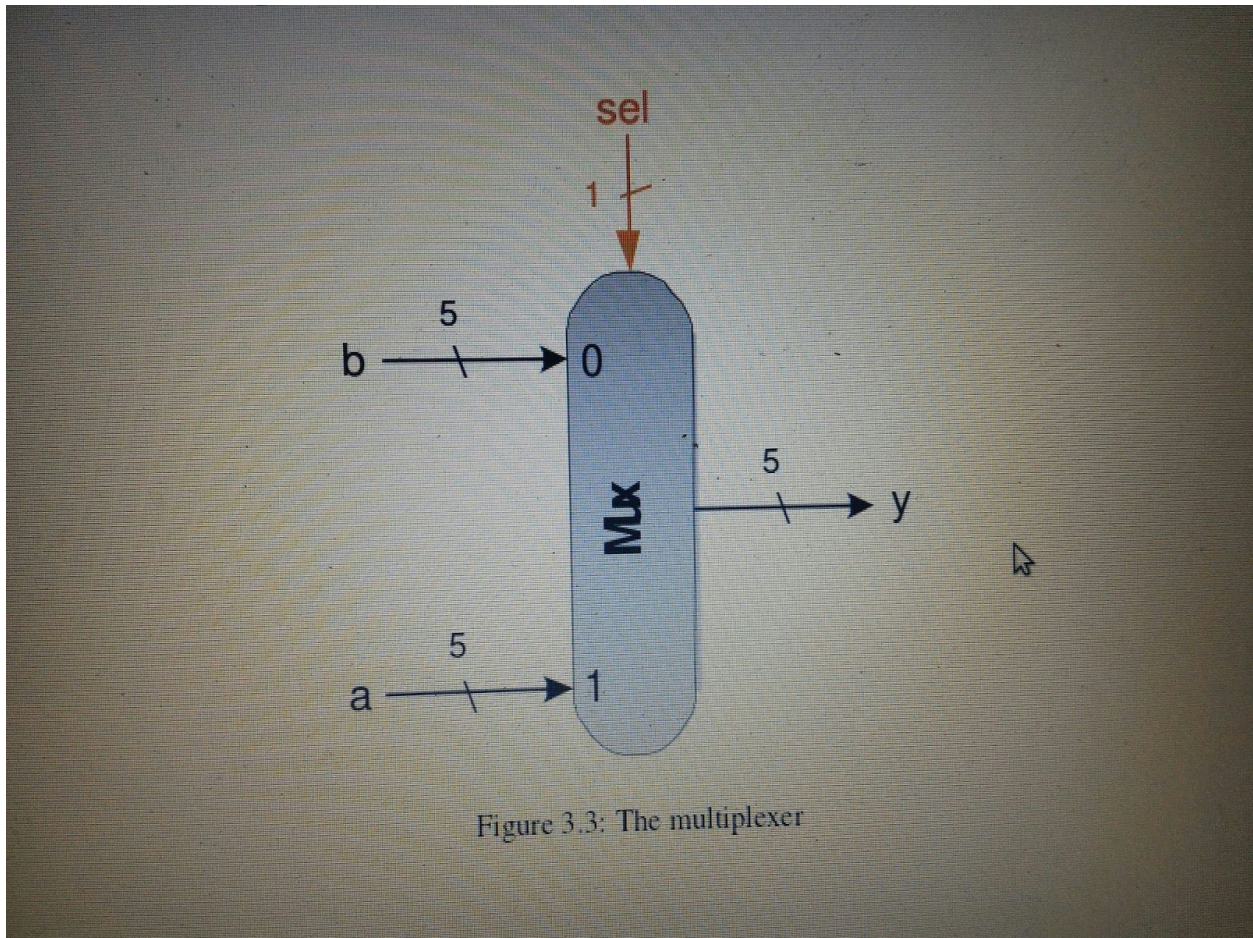


## Lab 3: Execution stage

In this lab, I just show the timing diagram, source code, and test bench of each component in the stage

1. Implementation
  - A. 32-bit Mux




```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////
// Company:
// Engineer: Hau Tao
// Create Date: 11:12:01 11/25/2015
// Module Name:    mux_32bit
////////////////////////////////////////////////////////////////
module mux_32bit(a,b,sel,y
);
input[31:0] a, b;
```

```
input sel;  
output[31:0] y;  
assign y = sel ? a: b;  
  
endmodule
```



## B. 5-bit mux

 


```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Engineer: Hau Tao
// Create Date: 09:44:04 11/16/2015
// Module Name:      mux_EX
/////////////////////////////////////////////////////////////////

module mux_EX( a, b, sel, y);
    input[4:0] a, b;
    input sel;
    output[4:0] y;
    assign y = sel ? a: b;
endmodule
```



### C. ALU control unit

 

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer: Hau Tao
//
// Create Date: 10:08:06 11/16/2015
/////////////////////////////////////////////////////////////////
module ALU_control_unit(input[5:0] function_bit, input[1:0] ALUOp, output reg[2:0] select
);
    //ALU op
    parameter LW = 2'b00;
    parameter SW = 2'b00;
    parameter branch_equal = 2'b01;
```

```

parameter R_type = 2'b10;
parameter not_valid = 2'b11;

//functionality
parameter loadword_func = 6'bxxxxxx;
parameter storeword_func = 6'bxxxxxx;
parameter branch_equal_func = 6'bxxxxxx;
parameter add_func = 6'b100000;
parameter subtract_func = 6'b100010;
parameter AND_func = 6'b100100;
parameter OR_func = 6'b100101;
parameter set_on_less_than_func = 6'b101010;

//alu_control_input
parameter ADD_control = 3'b010;
parameter SUBTRACT_control = 3'b110;
parameter OR_control = 3'b001;
parameter AND_control = 3'b000;
parameter SET_ON_LESS_THAN_control = 3'b111;
initial begin
    if( loadword_func == 6'bxxxxxx || storeword_func == 6'bxxxxxx)
        begin
            select = 3'b010;
        end

    else if (branch_equal_func == 6'bxxxxxx)
        begin
            select = 3'b110;
        end

    end
always@*
case (ALUop)
LW: select = ADD_control;
SW: select = ADD_control;

branch_equal: select = SUBTRACT_control;

R_type:begin

```

```

    case(function_bit)
    add_func: begin
    select = ADD_control;
    end


    subtract_func: begin
    select = SUBTRACT_control;
    end

    AND_func:  begin
    select = AND_control ;
    end
    OR_func: begin
    select = OR_control ;
    end
    set_on_less_than_func: begin
    elect = SET_ON_LESS_THAN_control ;
    end
    endcase
    end
    default: $display("Not available instruction");
    endcase
endmodule

```



#### D. ALU

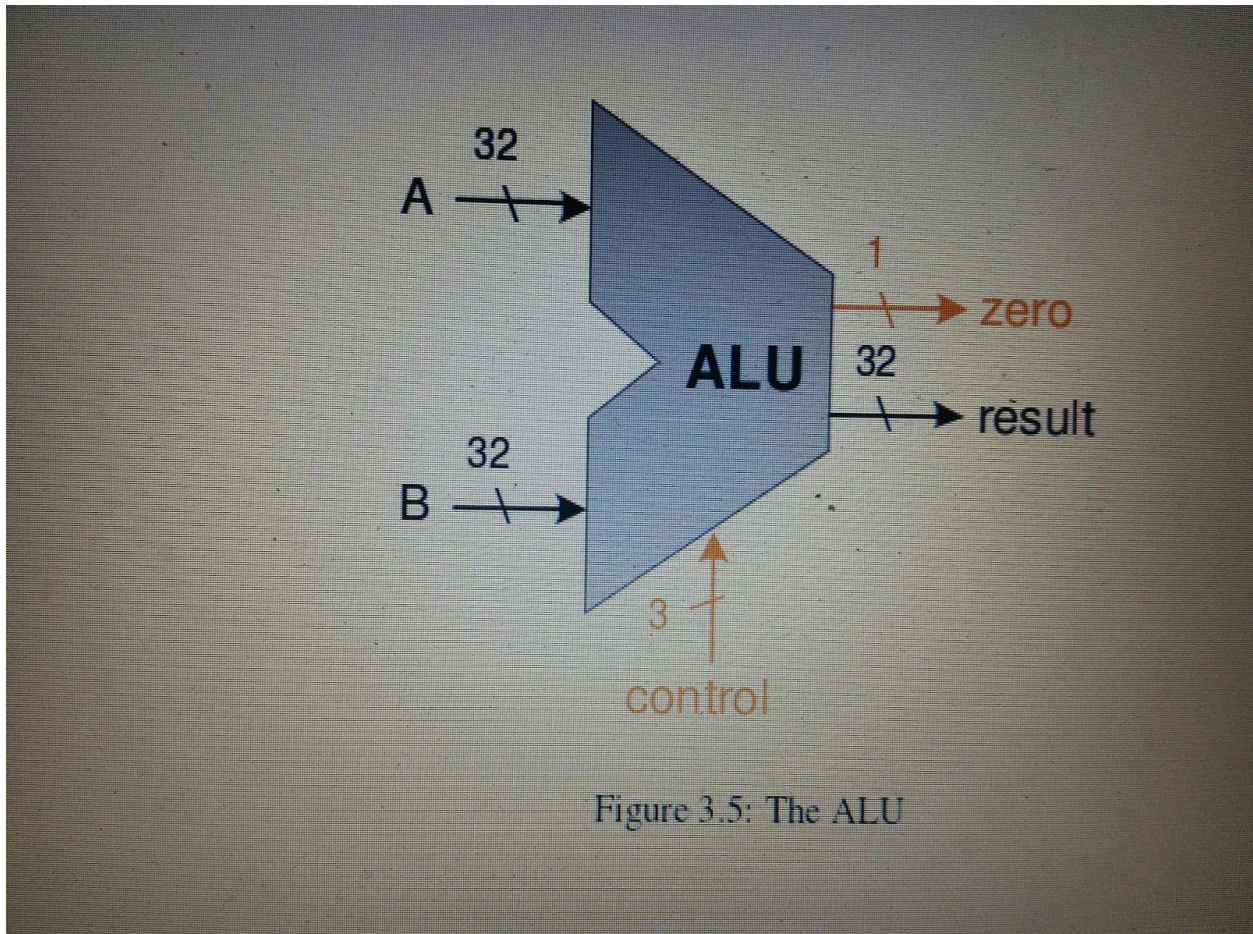

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer: Hau tao
//
// Create Date: 20:53:46 11/24/2015
// Module Name:    alu
/////////////////////////////////////////////////////////////////
module alu(
    input wire [31:0] A,
    input wire [31:0] B,
    input wire [2:0] control,
```

```

output reg          zero,
output reg [31:0] result
);

parameter add = 3'b010,
subtract = 3'b110,
and_alu = 3'b000,
or_alu = 3'b001,
set_on_less_than = 3'b111;


always @* begin
case (control)
add: result <= A + B;
subtract: result <= A - B;
and_alu: result <= A&B;
or_alu: result <= A|B;
set_on_less_than: result <= (A<B)? 1:0;
default: result <= 32'bx;
endcase
begin
if (result==0)
zero <=0;
end

end
endmodule

```



## E. Adder

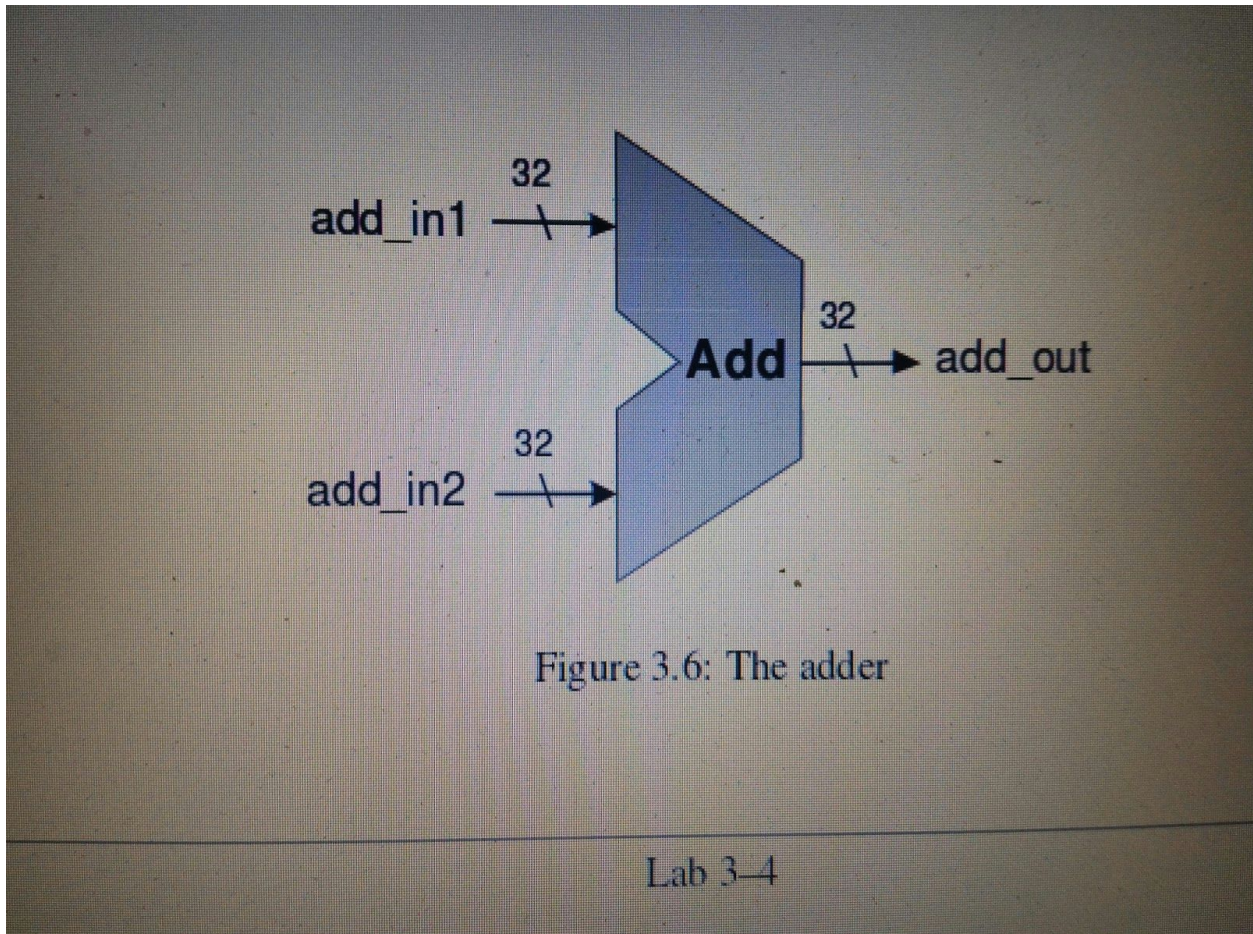

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Engineer: Hau Tao
//
// Create Date: 09:35:04 11/16/2015
// Module Name:      adder
/////////////////////////////////////////////////////////////////
module adder( input [31:0] add_in1, input[31:0] add_in2, output reg[31:0] add_out
    );
    always @ *
    begin
```

```
    add_out = add_in1 + add_in2;
end
```

```
endmodule
```

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer: hau Tao
//
// Create Date: 11:18:57 11/25/2015
/////////////////////////////////////////////////////////////////
module The_EX_stage(
    input [1:0] ctlwb_out,
    input [2:0] ctm_out,
    input [31:0] adder_out,
    input        aluzero,
    input [31:0] alu_out,
    input [31:0] readdat2,
    input [4:0] mux_out,

    output reg[1:0] wb_ctlout,
    output reg [2:0] m_ctlout,
    output reg [31:0] add_result,
    output reg        zero,
    output reg [31:0] alu_result,
    output reg [31:0] rdata2out,
    output reg [4:0] five_bit_muxout
);

always @*
begin
    #5 // clock cycle of the latch
    wb_ctlout <= ctlwb_out;
        m_ctlout <= ctm_out;
        add_result <= adder_out;
```


```
zero  <= aluzero;  
alu_result <= alu_out;  
rdata2out <= readdat2;  
five_bit_muxout<= mux_out;
```

```
end
```

```
endmodule
```



## F. EX latch

 

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer: hau Tao
//
// Create Date: 11:18:57 11/25/2015
/////////////////////////////////////////////////////////////////
module The_EX_stage(
    input [1:0] ctlwb_out,
    input [2:0] ctm_out,
    input [31:0] adder_out,
    input      aluzero,
    input [31:0] alu_out,
    input [31:0] readdat2,
    input [4:0] mux_out,
```

```

output reg[1:0] wb_ctlout,
output reg [2:0] m_ctlout,
output reg [31:0] add_result,
output reg      zero,
output reg [31:0] alu_result,
output reg [31:0] rdata2out,
output reg [4:0] five_bit_muxout
    );

```

```

always @*
begin
    #5 // clock cycle of the latch
    wb_ctlout <= ctlwb_out;
        m_ctlout <= ctlm_out;
        add_result <= adder_out;
        zero <= aluzero;
        alu_result <= alu_out;
        rdata2out <= readdat2;
        five_bit_muxout<= mux_out;

```

```

end

```

```

endmodule

```

## G. EX stage combination

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer: Hau Tao
//
// Create Date: 11:37:10 11/25/2015
// Design Name:
// Module Name:      EX_stage_combination
/////////////////////////////////////////////////////////////////
module EX_stage_combination(
    input [1:0] wb_ctlout,
    input [2:0] m_ctlout,
    input [3:0] ex_ctlout,
    input [31:0] npcout,
    input [31:0] rdata1out,
    input [31:0] rdata2out,
    input [31:0] s_extendout,
    input [4:0] instrout_2016,
    input [4:0] instrout_1511,

    output wire [1:0] EX_MEM_wb_ctlout,
    output wire [2:0] EX_MEM_m_ctlout,
    output wire [31:0] EX_MEM_add_result,
    output wire          EX_MEM_zero,
    output wire [31:0] EX_MEM_alu_result,
    output wire [31:0] EX_MEM_rdata2out,
    output wire [4:0] EX_MEM_five_bit_muxout
);
    wire [4:0] mux_5bit_output;
    wire [31:0] mux_32bit_output;
    wire [2:0] alu_input;
    wire alu_zero_output;
    wire [31:0] alu_result_output;
    wire [31:0] adder_output;

    mux_32bit my_mux_32bit (
        .a(s_extendout),
        .b(rdata2out),
```



```

        .sel(ex_ctlout[0]),
        .y(mux_32bit_output)
    );

    mux_EX my_mux_EX_5bit (
        .a(instrout_1511),
        .b(instrout_2016),
        .sel(ex_ctlout[3]),
        .y(mux_5bit_output)
    );

    ALU_control_unit my_alu_control_unit (
        .function_bit(s_extendout[5:0]),
        .ALUOp(ex_ctlout[2:1]),
        .select(alu_input)
    );

    alu my_alu (
        .A(rdata1out),
        .B(mux_32bit_output),
        .control(alu_input),
        .zero(alu_zero_output),
        .result(alu_result_output)
    );

    adder my_adder (
        .add_in1(npcout),
        .add_in2(s_extendout),
        .add_out(adder_output)
    );

    The_EX_stage EX_register (
        .ctlwb_out(wb_ctlout),
        .ctlm_out(m_ctlout),
        .adder_out(adder_output),
        .aluzero(alu_zero_output),
        .alu_out(alu_result_output),
        .readdat2(rdata2out),
        .mux_out(mux_5bit_output),
        .wb_ctlout(EX_MEM_wb_ctlout),
        .m_ctlout(EX_MEM_m_ctlout),
        .add_result(EX_MEM_add_result),
        .zero(EX_MEM_zero),

```

```
.alu_result(EX_MEM_alu_result),  
.rdata2out(EX_MEM_rdata2out),  
.five_bit_muxout(EX_MEM_five_bit_muxout)  
);
```

```
endmodule
```

## 2. Test Bench

### A. 32-bit Mux

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer: Hau Tao
```

```
//
```

```
// Create Date: 11:13:30 11/25/2015
```

```
// Design Name: mux_32bit
```

```
// Module Name: /home/hau/Desktop/lab3/test_mux_32bit.v
```

```
// Project Name: lab3
```

```
////////////////////////////////////////////////////////////////
```

```
module test_mux_32bit;
```

```
    // Inputs
```

```
    reg [31:0] a;
```

```
    reg [31:0] b;
```

```
    reg sel;
```

```
    // Outputs
```

```
    wire [31:0] y;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    mux_32bit uut (
```

```
        .a(a),
```

```
        .b(b),
```

```
        .sel(sel),
```

```
        .y(y)
```

```
    );
```

```
    initial begin
```

```
        a = 32'b01010;
```

```
        b = 32'b10101;
```

```
        sel = 1'b1;
```

```
        #10;
```

```
        a = 32'b000000;
```



```

#10
sel = 1'b1;
#10;
b = 32'b11111;
#5;
a = 32'b00101;
#5;
sel = 1'b0;
b = 32'b11101;
#5;
sel = 1'bx;
end
always @(a or b or sel)

#1 $display("At t = %0d sel =%b a =%b b=%b y=%b", $time, sel, a, b, y);

endmodule

```

## B. 5-bit Mux

`timescale 1ns / 1ps

//

// Company:

// Engineer: Hau Tao

//

// Create Date: 09:59:42 11/16/2015

// Design Name: mux\_EX

// Module Name: /home/hau/Desktop/lab3/test\_mux\_EX.v

//

module test\_mux\_EX;

// Inputs

reg [4:0] a;

reg [4:0] b;

reg sel;

// Outputs

wire [4:0] y;

// Instantiate the Unit Under Test (UUT)

mux\_EX uut (

.a(a),

.b(b),

.sel(sel),

.y(y)

);

initial begin

a = 5'b01010;

b = 5'b10101;

sel = 1'b1;

#10;

a = 5'b00000;

#10

sel = 1'b1;

```
#10;
b = 5'b11111;
#5;
a= 5'b00101;
#5;
sel = 1'b0;
b = 5'b11101;
#5;
sel = 1'bx;
    end
always @(a or b or sel)

#1 $display("At t = %0d sel =%b a =%b b=%b y=%b",$time, sel, a, b, y);
```

```
endmodule
```

### C. ALU control unit

`timescale 1ns / 1ps

//

// Engineer: Hau Tao

// Create Date: 11:27:34 11/23/2015

// Design Name: ALU\_control\_unit

// Project Name: lab3

//

module test\_alu\_control\_unit;

// Inputs

reg [5:0] function\_bit;

reg [1:0] ALUop;

// Outputs

wire [2:0] select;

// Instantiate the Unit Under Test (UUT)

ALU\_control\_unit uut (

    .function\_bit(function\_bit),

    .ALUop(ALUop),

    .select(select)

);

initial begin

    // Initialize Inputs

    function\_bit = 6'b100000;

    ALUop = 2'b00;

    \$monitor("ALUop = %b\t function\_bit = %b\t select = %b", ALUop, function\_bit, select);

    #1

    ALUop = 2'b01;

    function\_bit = 6'b100000;

    #1

    ALUop = 2'b10;

    function\_bit = 6'b100000;



```
#1
function_bit = 6'b100010;
#1
function_bit = 6'b100100;
#1
function_bit = 6'b100101;
#1
function_bit = 6'b101010;
#1
$finish;
end
```

```
endmodule
```

#### D. ALU

`timescale 1ns / 1ps

```
////////////////////////////////////  
// Company:  
// Engineer:hau tao  
// Create Date: 21:13:13 11/24/2015  
// Design Name: alu  
////////////////////////////////////
```

module test\_alu;

```
    // Inputs  
    reg [31:0] A;  
    reg [31:0] B;  
    reg [2:0] control;
```

```
    // Outputs  
    wire zero;  
    wire [31:0] result;
```

// Instantiate the Unit Under Test (UUT)

```
alu uut (  
    .A(A),  
    .B(B),  
    .control(control),  
    .zero(zero),  
    .result(result)  
);
```

initial begin

```
    // Initialize Inputs  
    A <= 'b1010;  
    B <= 'b0111;  
    control <= 'b011;  
    $display("A=%b\tB=%b",A,B);  
    $monitor("ALUOp=%b\tresult=%b",control, result);  
    #1
```

```
control <= 'b100;  
#1  
control <= 'b010;  
#1  
control <= 'b111;  
#1  
control <= 'b011;  
#1  
control <= 'b110;  
#1  
control <= 'b001;  
#1  
control <= 'b000;  
#1  
$finish;
```

```
end
```

```
endmodule
```

E. Adder

`timescale 1ns / 1ps

```
////////////////////////////////////  
// Engineer: Hau Tao  
//  
// Create Date: 09:39:54 11/16/2015  
// Design Name: adder  
// Module Name: /home/hau/Desktop/lab3/test_adder.v  
// Project Name: lab3  
////////////////////////////////////
```

```
module test_adder;
```

```
    // Inputs
```

```
    reg [31:0] add_in1;
```

```
    reg [31:0] add_in2;
```

```
    // Outputs
```

```
    wire [31:0] add_out;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    adder uut (
```

```
        .add_in1(add_in1),
```

```
        .add_in2(add_in2),
```

```
        .add_out(add_out)
```

```
    );
```

```
    initial begin
```

```
        // Initialize Inputs
```

```
        add_in1 = 0;
```

```
        add_in2 = 0;
```

```
        // Wait 100 ns for global reset to finish
```

```
        #10;
```

```
        add_in1 = 5;
```

```
        add_in2 = 12;
```



```
// Add stimulus here
#2
$display("time = %0d\tadd_in1=%0d\t add_in2=%0d\tadd_out=%0d\t", $time, add_in1,
add_in2, add_out);

end

endmodule
```

E.EX latch

`timescale 1ns / 1ps

//

// Company:

// Engineer: Hau Tao

//

// Create Date: 18:21:21 11/25/2015

// Design Name: The\_EX\_stage

// Module Name: /home/hau/Desktop/lab3/testing\_EX\_latch.v

//

module testing\_EX\_latch;

// Inputs

reg [1:0] ctlwb\_out;

reg [2:0] ctm\_out;

reg [31:0] adder\_out;

reg aluzero;

reg [31:0] alu\_out;

reg [31:0] readdat2;

reg [4:0] mux\_out;

// Outputs

wire [1:0] wb\_ctlout;

wire [2:0] m\_ctlout;

wire [31:0] add\_result;

wire zero;

wire [31:0] alu\_result;

wire [31:0] rdata2out;

wire [4:0] five\_bit\_muxout;

// Instantiate the Unit Under Test (UUT)

The\_EX\_stage uut (

.ctlwb\_out(ctlwb\_out),

.ctm\_out(ctm\_out),

.adder\_out(adder\_out),

.aluzero(aluzero),

```
.alu_out(alu_out),  
.readdat2(readdat2),  
.mux_out(mux_out),  
.wb_ctlout(wb_ctlout),  
.m_ctlout(m_ctlout),  
.add_result(add_result),  
.zero(zero),  
.alu_result(alu_result),  
.rdata2out(rdata2out),  
.five_bit_muxout(five_bit_muxout)  
);
```

```
initial begin
```

```
    // Initialize Inputs
```

```
    ctlwb_out = 0;
```

```
    ctlm_out = 0;
```

```
    adder_out = 0;
```

```
    aluzero = 0;
```

```
    alu_out = 0;
```

```
    readdat2 = 0;
```

```
    mux_out = 0;
```

```
#10
```

```
    ctlwb_out = 1;
```

```
    ctlm_out = 2;
```

```
    adder_out = 3;
```

```
    aluzero = 0;
```

```
    alu_out = 5;
```

```
    readdat2 = 6;
```


```
    mux_out = 7;
```

```
end
```

```
endmodule
```

### 3. Simulation

#### A. 32-bit mux

 

At t = 1 sel = 1 a = 000000000000000000000000000000001010

b = 0000000000000000000000000000000010101 y = 000000000000000000000000000000001010

At t = 11 sel = 1 a = 00000000000000000000000000000000

b = 0000000000000000000000000000000010101 y = 00000000000000000000000000000000

At t = 31 sel = 1 a = 00000000000000000000000000000000

b = 0000000000000000000000000000000011111 y = 00000000000000000000000000000000

At t = 36 sel = 1 a = 00000000000000000000000000000000101

b = 0000000000000000000000000000000011111 y = 00000000000000000000000000000000101

At t = 41 sel = 0 a = 00000000000000000000000000000000101


b = 0000000000000000000000000000000011101 y = 0000000000000000000000000000000011101

At t = 46 sel = x a = 00000000000000000000000000000000101

b = 0000000000000000000000000000000011101 y = 00000000000000000000000000000000xx101



## B. 5-bit mux

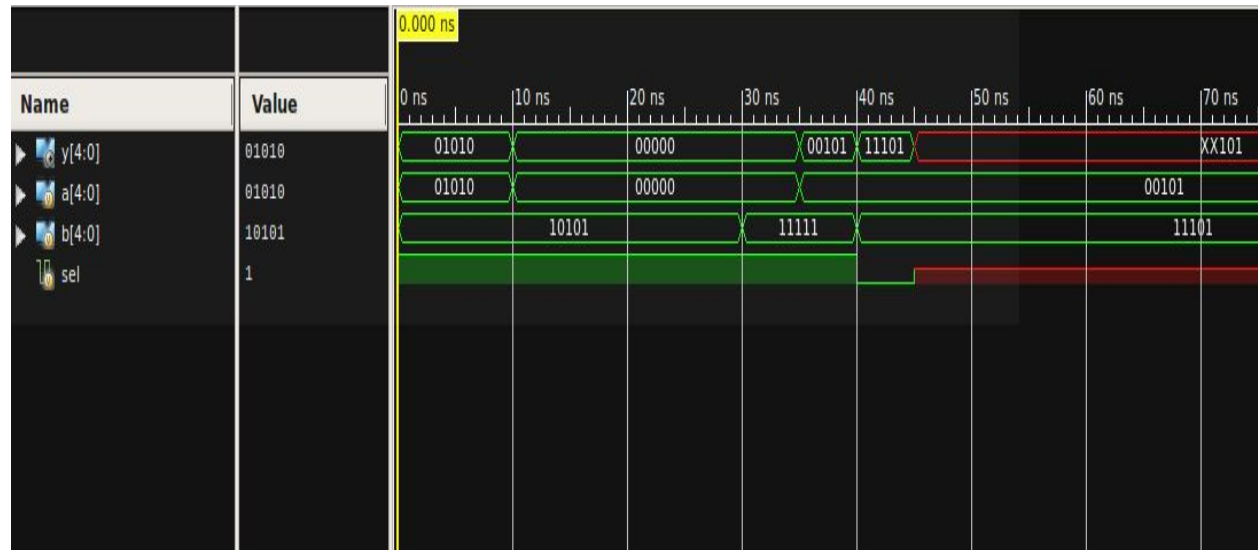

At t = 11 sel = 1 a = 00000 b = 10101 y = 00000


At t = 31 sel = 1 a = 00000 b = 11111 y = 00000

At t = 36 sel = 1 a = 00101 b = 11111 y = 00101

At t = 41 sel = 0 a = 00101 b = 11101 y = 11101

At t = 46 sel = x a = 00101 b = 11101 y = xx101

## C.alu control unit

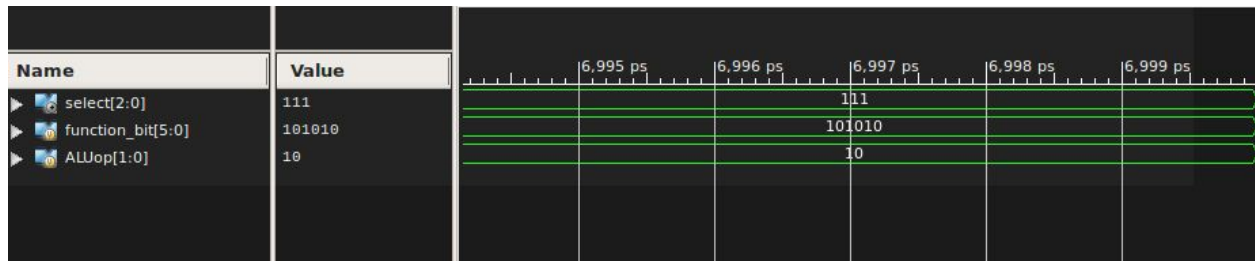


ALUop =10     function\_bit =100010select=110

ALUop =10     function\_bit =100100select=000

ALUop =10     function\_bit =100101select=001

ALUop =10     function\_bit =101010select=111

## D. ALU

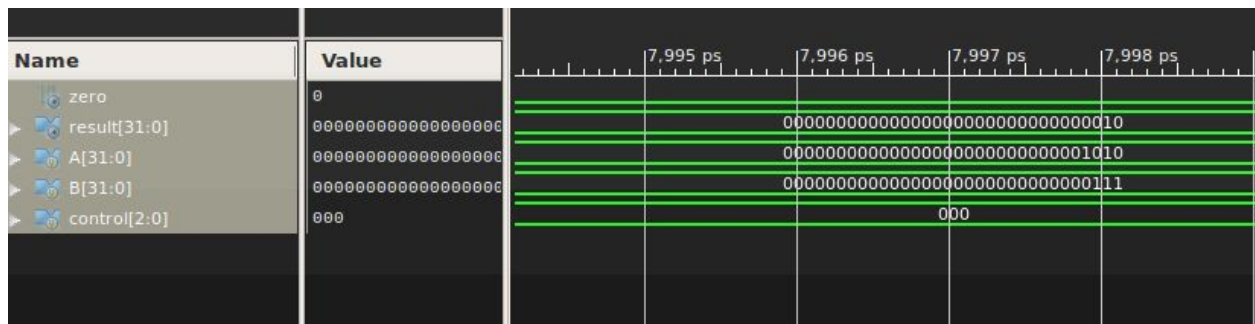

ALUOp=011     result=xx

ALUOp=100     result=xx

ALUOp=010     result=0000000000000000000000000000000010001

ALUOp=111     result=00


ALUOp=011     result=xx

ALUOp=110     result=0011

ALUOp=001     result=001111

ALUOp=000     result=0010

## E. Adder

 

time = 12     add\_in1=5     add\_in2=12     add\_out=17

## F. EX latch

Name		Value	999,992 ps	999,993 ps	999,994 ps	999,995 ps	999,996 ps
wb_ctlout[1:0]	1					1	
m_ctlout[2:0]	2					2	
add_result[31:0]	3					3	
zero	0						
alu_result[31:0]	5					5	
rdata2out[31:0]	6					6	
five_bit_muxout[4:0]	7					7	
ctlwb_out[1:0]	1					1	
ctlm_out[2:0]	2					2	
adder_out[31:0]	3					3	
aluzero	0						
alu_out[31:0]	5					5	
readdat2[31:0]	6					6	
mux_out[4:0]	7					7	

It's hard to test entire ex stage separately. As a mention of professor, I will test it when connecting all stages together