

## Lab 4: Memory stage

In this lab , I just show source code, testbench and simulation

## A.Implementation

## 1. data memory

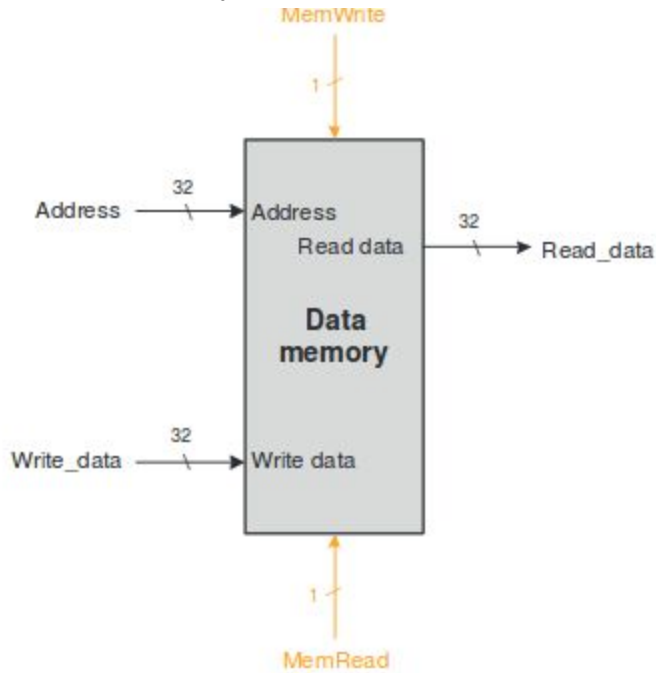


Figure 4.3: The data memory unit

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////

// Engineer: hau tao
//
// Create Date:01:50:27 12/06/2015
// Design Name:
// Module Name:    data_mem

/////////////////////////////////////////////////////////////////

module data_mem(input [31:0] address, inout[31:0] writedata, input memread, input memwrite,
output reg[31:0] readdata
);
  reg[31:0] register[0:255];
  reg [31:0] data_in;

```

```

integer i;
initial
begin
    data_in <= 'h0000000A;
    register[0] <= 'h002300AA;
    register[1] <= 'h10654321;
    register[2] <= 'h00100022;
    register[3] <= 'h8C123456;
    register[4] <= 'h8F123456;

    register[5] <= 'hAD654321;
    register[6] <= 'h13012345;
    register[7] <= 'hAC654321;
    register[8] <= 'h12012345;
    for ( i = 9; i < 255; i = i + 1)
        begin
            register[i] <= 'h11111111;
        end
    end
    assign writedata = (memread)? data_in:'hx;
    // write data
    always @ (address or writedata)

        begin
            if ( memwrite) begin
                register[address] = writedata;
            end

            //read data
            if ( memread) begin
                readdata = register[address] ;
            end
        end
end

endmodule

```

## 2. And gate



Figure 4.2: The and gate

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer: hau tao
//
// Create Date:13:48:16 12/06/2015
// Design Name:
// Module Name:    and_gate
/////////////////////////////////////////////////////////////////
module and_gate( input zero, input branch, output reg PCSrc
);
    always @*
    begin
        PCSrc = branch & zero;
    end

endmodule
```

### 3. Memory latch

 


Figure 4.4: The MEM/WB pipeline register (latch)


```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////
// Company:
// Engineer: hau tao
//
// Create Date:14:01:42 12/06/2015
// Design Name:
// Module Name:      mem_latch
////////////////////////////////////////////////////////////////
module mem_latch(input [1:0] control_wb_in, input[31:0] Read_data_in, input[31:0]
ALU_result_in, input[4:0] Write_reg_in,
output reg[1:0]mem_control_wb, output reg[31:0]Read_data, output reg[31:0]mem_ALU_result,
output reg[4:0] mem_Write_reg
);

always @*
begin
    #5 // clock cycle of the latch
    mem_control_wb <= control_wb_in;
    Read_data <= Read_data_in;
    mem_ALU_result <= ALU_result_in;
    mem_Write_reg <= Write_reg_in;

end
```

endmodule

#### 4. memory stage connection

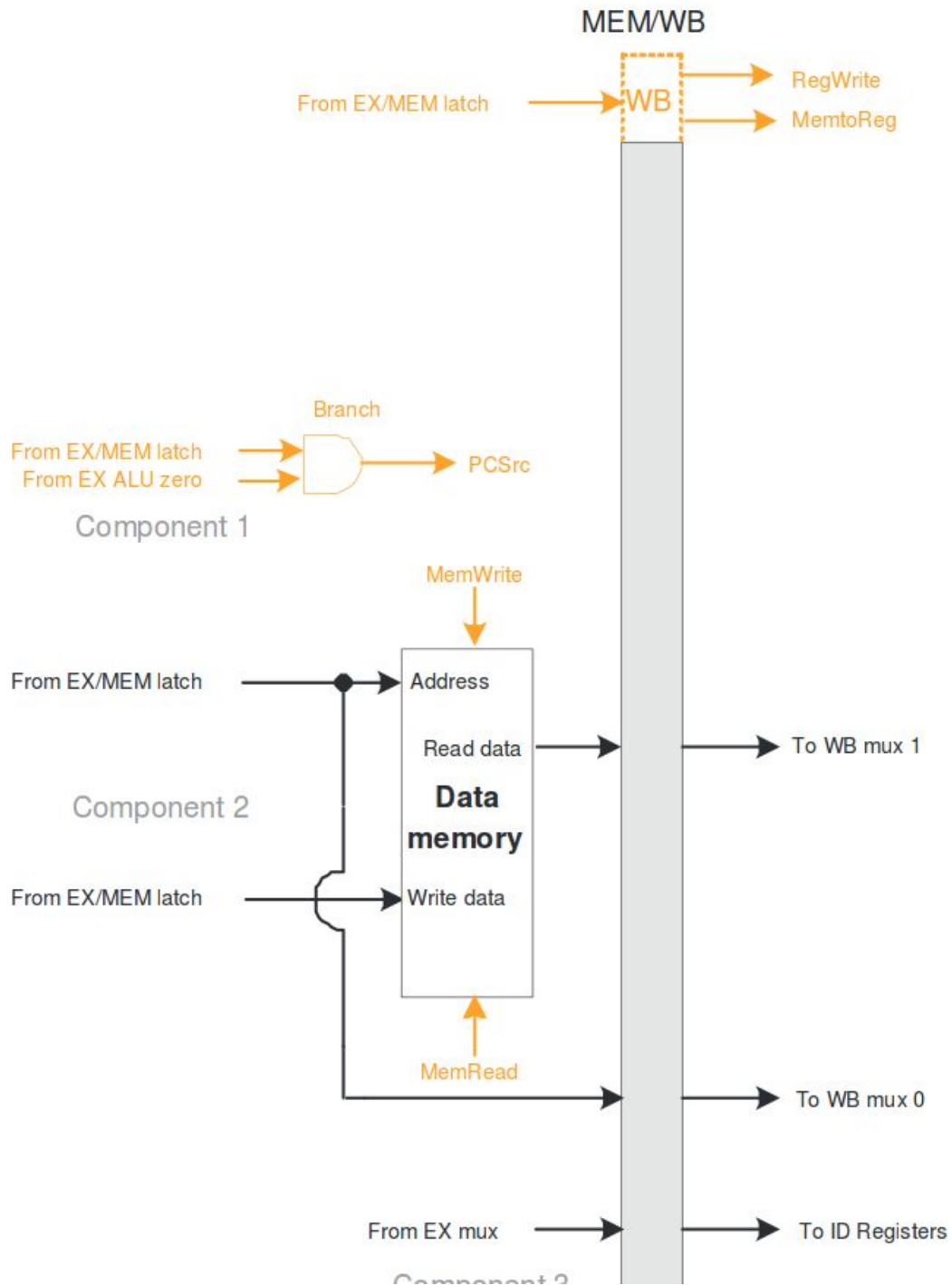

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////
// Engineer: hau tao
//
// Create Date: 14:18:46 12/06/2015
// Design Name:
// Module Name:      memory_stage_connection

////////////////////////////////////////////////////////////////
module memory_stage_connection(input [1:0] control_wb_in, input [2:0] ex_mem_latch, input
zero, input[31:0] ALU_result_in,
inout[31:0] To_mem_write_data, input[31:0] Write_reg_in, output
wire[1:0]mem_control_wb,output wire[31:0] Read_data, output wire[31:0]mem_ALU_result,
output wire[4:0] mem_Write_reg
);
    wire PCSrc;

    wire [31:0] Read_data_in;
    and_gate and_gate_1 (
        .zero(zero),
        .branch(ex_mem_latch[2]),
        .PCSrc(PCSrc)
    );
    data_mem data_mem_1 (
        .address(ALU_result_in),
        .writedata(To_mem_write_data),
        .memread(ex_mem_latch[1]),
        .memwrite(ex_mem_latch[0]),
        .readdata(Read_data_in)
    );
    mem_latch mem_latch_1 (
        .control_wb_in(control_wb_in),
        .Read_data_in(Read_data_in),
        .ALU_result_in(ALU_result_in),
        .Write_reg_in(Write_reg_in),
        .mem_control_wb(mem_control_wb),
        .Read_data(Read_data),
        .mem_ALU_result(mem_ALU_result),
        .mem_Write_reg(mem_Write_reg)
    );

```

endmodule

## B. Test bench

### 1. data memory

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer: hau tao
```

```
//
```

```
// Create Date: 13:05:11 12/06/2015
```

```
// Design Name: data_mem
```

```
// Module Name: /home/hau/Desktop/lab4/test_mem_data.v
```

```
// Project Name: lab4
```

```
////////////////////////////////////////////////////////////////
```

```
module test_mem_data;
```

```
    // Inputs
```

```
    reg [31:0] address;
```

```
    reg memread;
```

```
    reg memwrite;
```

```
    // Outputs
```

```
    wire [31:0] readdata;
```

```
    // Bidirs
```

```
    wire [31:0] writedata;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    data_mem uut (
```

```
        .address(address),
```

```
        .writedata(writedata),
```

```
        .memread(memread),
```

```
        .memwrite(memwrite),
```

```
        .readdata(readdata)
```

```
    );
```

```
    initial begin
```

```
        // Initialize Inputs
```

```
        address = 0;
```

```
        memread = 0;
```

```
        memwrite = 0;
```



```

// Wait 100 ns for global reset to finish

#1;

memread =1;
#1;
memwrite =1;
#1;
address =1;
#1;
address =2;
#1
address =3;
memwrite =0;
#1
address =4;

#1
address =5;
#1
address =6;
end

// Add stimulus here
always@(address or memread or memwrite)begin
#1

$display("time=%0d\taddress=%0d\twritedata=%h\treaddata=%h",$time,address,writedata,read
data);
end

endmodule

```

2. and gate  
timescale 1ns / 1ps

```
////////////////////////////////////  
// Company:  
// Engineer: hau tao  
//  
// Create Date: 13:53:06 12/06/2015  
// Design Name: and_gate  
// Module Name: /home/hau/Desktop/lab4/test_gate.v  
// Project Name: lab4  
////////////////////////////////////
```

```
module test_gate;
```

```
    // Inputs  
    reg zero;  
    reg branch;
```

```
    // Outputs  
    wire PCSrc;
```

```
    // Instantiate the Unit Under Test (UUT)  
    and_gate uut (  
        .zero(zero),  
        .branch(branch),  
        .PCSrc(PCSrc)  
    );
```

```
    initial begin  
        // Initialize Inputs  
        zero = 0;  
        branch = 0;  
  
        // Wait 100 ns for global reset to finish  
  
        #1;  
        branch = 1;  
        #1  
        zero = 1;  
        #1  
        branch = 0;
```

```

        end

        always @* begin

            #2$display("time=%0d\tbranch=%0b\tzero=%0b\tPCSrc=%0b\t", $time, branch, zero,
PCSrc);

        end

```

```
endmodule
```

```
3. memory latch
```

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////
```

```
// Company:
```

```
// Engineer: hau tao
```

```
//
```

```
// Create Date: 14:16:05 12/06/2015
```

```
// Design Name: mem_latch
```

```
// Module Name: /home/hau/Desktop/lab4/test_mem_latch.v
```

```
// Project Name: lab4
```

```
////////////////////////////////////
```

```
module test_mem_latch;
```

```
    // Inputs
```

```
    reg [1:0] control_wb_in;
```

```
    reg [31:0] Read_data_in;
```

```
    reg [31:0] ALU_result_in;
```

```
    reg [4:0] Write_reg_in;
```

```
    // Outputs
```

```
    wire [1:0] mem_control_wb;
```

```
    wire [31:0] Read_data;
```

```
    wire [31:0] mem_ALU_result;
```

```
    wire [4:0] mem_Write_reg;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    mem_latch uut (
```

```
        .control_wb_in(control_wb_in),
```

```
.Read_data_in(Read_data_in),  
.ALU_result_in(ALU_result_in),  
.Write_reg_in(Write_reg_in),  
.mem_control_wb(mem_control_wb),  
.Read_data(Read_data),  
.mem_ALU_result(mem_ALU_result),  
.mem_Write_reg(mem_Write_reg)  
);
```

```
initial begin
```

```
    // Initialize Inputs
```

```
    control_wb_in = 0;
```

```
    Read_data_in = 0;
```

```
    ALU_result_in = 0;
```

```
    Write_reg_in = 0;
```

```
    // Wait 100 ns for global reset to finish
```

```
    #1;
```

```
    control_wb_in = 1;
```

```
    Read_data_in = 2;
```

```
    ALU_result_in = 3;
```

```
    Write_reg_in = 4;
```


```
    // Add stimulus here
```

```
end
```

```
endmodule
```


## C. Simulation

### 1. data memory

 

time=1	address=0	writedata=xxxxxxxx	readdata=xxxxxxxx
time=3	address=1	writedata=0000000a	readdata=002300aa
time=5	address=3	writedata=0000000a	readdata=0000000a
time=7	address=5	writedata=0000000a	readdata=8c123456
time=9	address=6	writedata=0000000a	readdata=13012345

### 2. and gate

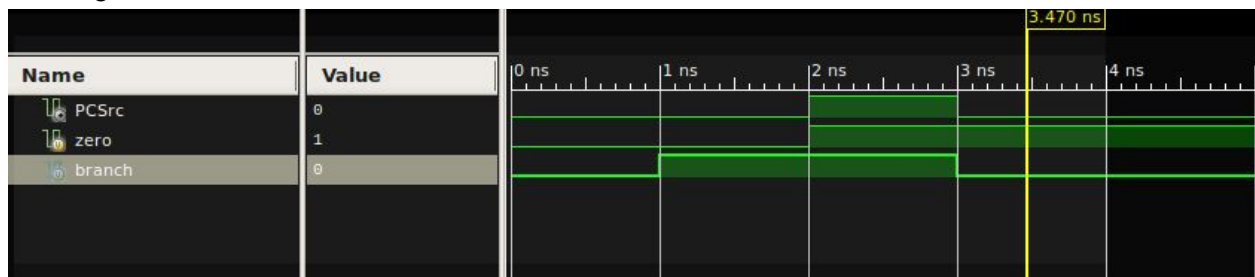

time=2	branch=1	zero=0	PCSrc=0
time=4	branch=0	zero=1	PCSrc=0

3. memory latch

Name	Value	999,992 ps	999,993 ps	999,994 ps	999,995 ps	999,996 ps
mem_control_wb[1:0]	1				1	
Read_data[31:0]	2				2	
mem_ALU_result[31:0]	3				3	
mem_Write_reg[4:0]	4				4	
control_wb_in[1:0]	1				1	
Read_data_in[31:0]	2				2	
ALU_result_in[31:0]	3				3	
Write_reg_in[4:0]	4				4	