

Lab 2: The MIPS datapath in Verilog: The ID stage

A. Introduction

The objective of this lab is to implement and test the instruction decoder (ID) pipeline stage of the MIPS five stages pipeline. In this lab, I build up and test successfully 4 components of ID stages including control, register, sign extend, and ID latch.

B. Interface

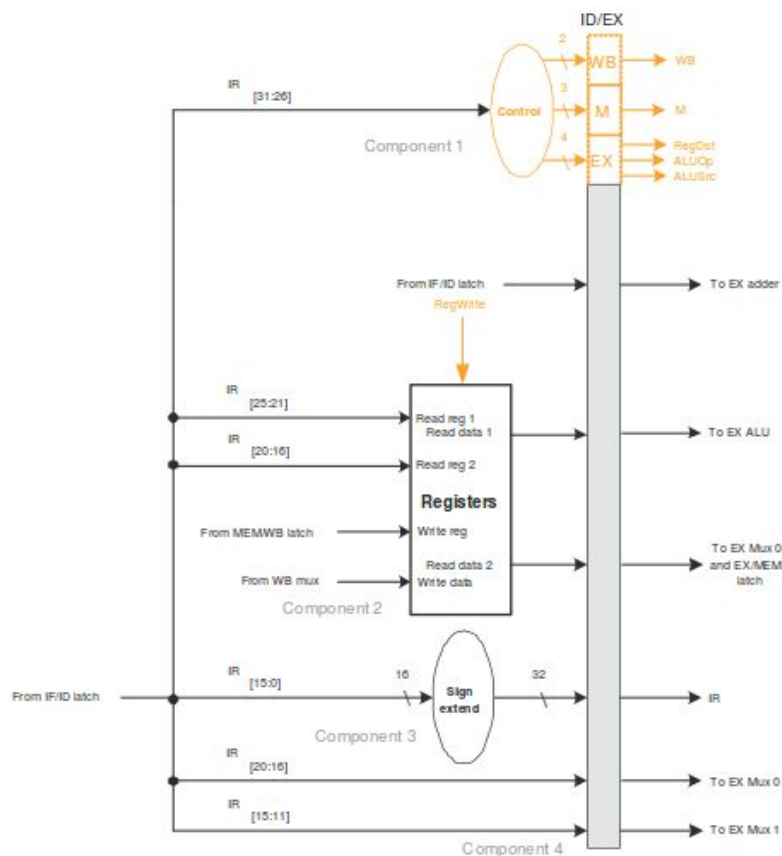


Figure 2.1: The ID stage

The Instruction decode (ID) stage figures it out that what instructions say to do and get the value from the registers, and the control unit will define what the output is . These outputs include 3 signals: M, WB, EX. We also need a sign extended unit to extend from 16 to 32-bit output

C. Design

The module I_DECODE instantiates the modules CONTROL, REG, S_EXTEND, and ID_EX

- The CONTROL module has input the opcode field of the IF_ID instr and output is the 9-bit control bits which are shown in figure which are shown in figure 2.2
- .The register file REG, which has 32 general purpose registers, and has input the rs and rt fields of IF_ID_ instr, MEM_WB_Writereg, MEM_WB_Writedata, and RegWrite (for the time being it can be from anywhere). Outputs are the contents of register rs and register rt.
- The combinational module S_EXTEND receives as input the 16-bit immediate field of IF_ID_instr and output is the 32 bit sign-extended value.
- The ID_EX module includes the pipeline register ID/EX and inputs the outputs of the CONTROL, REG, S_EXTEND modules, as well as the IF_ID_NPC, IF_ID_Instr[20-16] and IF_ID_Instr[15-11]. Outputs are the control bits (9 bits) NPC, Reg[rs], Reg[rt],signExtended (32 bit), Instr[20-16], and Instr[15-11].

Instruction	Execution/Address Calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Branch	Mem Read	Mem Write	Reg Write	Mem to Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X

Figure 2.2: ALUOp Control Bit and Function Code Sets (after [4])

The content of the register

002300AA

10654321

00100022

8C123456

8F123456

AD654321

13012345

AC654321

12012345

The sign-extended unit

 


Figure 2.3: The sign-extend unit

```
`timescale 1ns / 1ps
```

[illegible]

```

// Inputs
reg [15:0] unextended_signal;

// Outputs
wire [31:0] extended_signal;

// Instantiate the Unit Under Test (UUT)
extended_register uut (
    .unextended_signal(unextended_signal),
    .extended_signal(extended_signal)
);

initial begin
    // Initialize Inputs
    unextended_signal = 0;

    // Wait 1ns for global reset to finish

    #2 unextended_signal = 16'b1110000100111111;
    #3 unextended_signal = 16'b0000000100111111;
end
// Add stimulus here
always @*
begin
    #2 $display("Time = %0d\t unextended_signal =%0b\t
extended_signal=%0b\t", $time, unextended_signal, extended_signal);
    #1 $display("Time = %0d\t unextended_signal =%0b\t
extended_signal=%0b\t", $time, unextended_signal, extended_signal);
end
endmodule

```

- The control unit

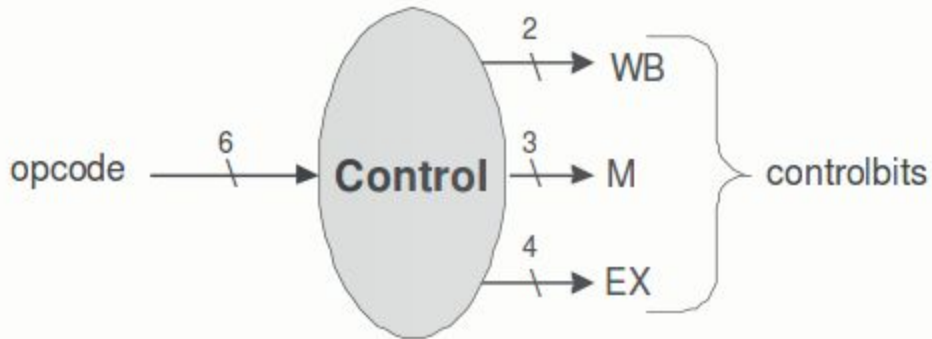


Figure 2.4: The control unit

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Engineer: Hau Tao
```

```
//
```

```
// Create Date: 14:35:07 11/07/2015
```

```
// Design Name: control_bit
```

```
// Module Name: /home/hau/Desktop/labcse401/lab2/ID_stage/test_control_bit.v
```

```
// Project Name: ID_stage
```

```
////////////////////////////////////////////////////////////////
```

```
module test_control_bit;
```

```
    // Inputs
```

```
    reg [5:0] opcode;
```

```
    // Outputs
```

```
    wire [3:0] EX;
```

```
    wire [2:0] MEM;
```

```

wire [1:0] WB;

// Instantiate the Unit Under Test (UUT)
control_bit uut (
    .opcode(opcode),
    .EX(EX),
    .MEM(MEM),
    .WB(WB)
);

initial begin
    // Initialize Inputs
    opcode = 6'b000000;
    #2 opcode = 6'b100011;
    #4 opcode = 6'b101011;
    #6 opcode = 6'b000100;
end

always @*
begin
    #2 $display("Time = %0d\t opcode = %0b\t EX = %0b\t MEM = %0b\t WB = %0b\t", $time,
opcode, EX, MEM, WB);
    #4 $display("Time = %0d\t opcode = %0b\t EX = %0b\t MEM = %0b\t WB = %0b\t", $time,
opcode, EX, MEM, WB);
    #6 $display("Time = %0d\t opcode = %0b\t EX = %0b\t MEM = %2b\t WB = %0b\t", $time,
opcode, EX, MEM, WB);
    #4 $display("Time = %0d\t opcode = %0b\t EX = %0b\t MEM = %0b\t WB = %0b\t", $time,
opcode, EX, MEM, WB);
end

endmodule

```


- The register File

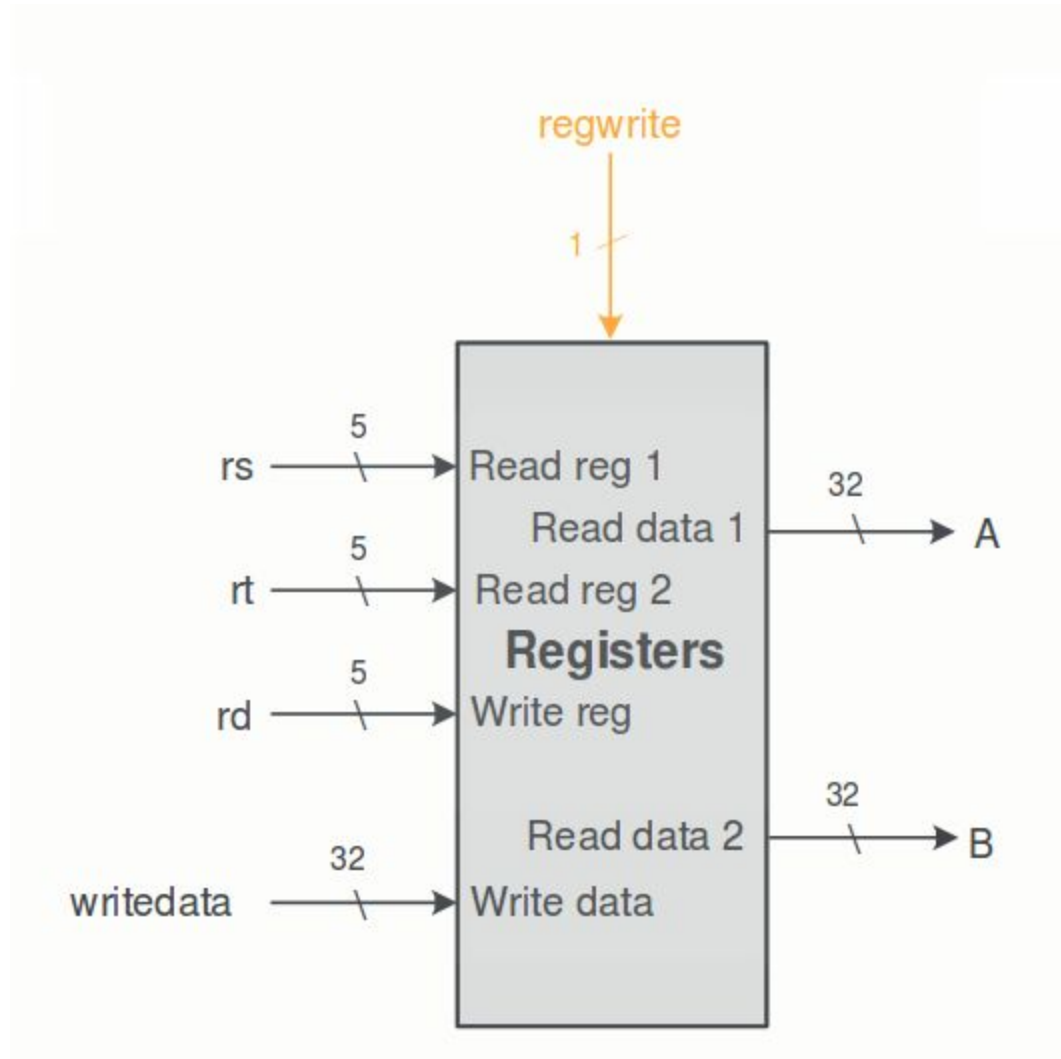


Figure 2.5: The register file

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////
```

```
// Company:
```

```
// Engineer: hau tao
//
// Create Date: 15:34:02 11/07/2015
// Design Name: register_file
// Module Name: /home/hau/Desktop/labcse401/lab2/ID_stage/test_reg.v
// Project Name: ID_stage
////////////////////////////////////////////////////////////////
```

```
module test_reg;
```

```
    // Inputs
```

```
    reg reg_write;
    reg [4:0] rs;
    reg [4:0] rt;
    reg [4:0] rd;
    reg [31:0] write_data;
    reg [31:0] register[0:4];
```

```
    integer i;
```

```
    // Outputs
```

```
    wire [31:0] A;
    wire [31:0] B;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    register_file uut (
        .reg_write(reg_write),
        .rs(rs),
        .rt(rt),
        .rd(rd),
        .write_data(write_data),
        .A(A),
        .B(B)
    );
```

```
    initial begin
```

```
        // Initialize Inputs
        register[0] <= 'h002300AA;
        register[1] <= 'h10654321;
```

```
register[2] <= 'h00100022;
```

```
// 2ns delay
```

```
#2
```

```
begin
```

```
reg_write = 1;
```

```
rs = 1;
```

```
rt = 2;
```

```
rd = 2;
```

```
write_data = 5;
```

```
end
```

```
end
```

```
always@*
```

```
begin
```

```
#3 $display("Time = %0d\t rs =%0h\t rt=%0h\t rd=%0h\t write_data=%0h\t register[rd]  
=%0h\t A=%0h\t B=%1h\t", $time, rs, rt, rd, write_data,register[rd], A, B);
```

```
end
```

- The ID/EX latch

 


Figure 2.6: The ID/EX pipeline register (latch)

```
module ID_latch (
    input[1:0] ctlwb_out,
    input[2:0] ctm_out,
    input[3:0] ctlex_out,
    input[31:0] npc,
    input[31:0] readdat1,
    input[31:0] readdat2,
    input[31:0] signext_out,
    input[4:0] instr_2016,
    input[4:0] instr_1511,

    output reg[1:0] wb_ctlout,
```

```

output reg[2:0] m_ctlout,
    output reg[3:0] ex_ctlout,
output reg[31:0] npcout,
output reg[31:0] rdata1out,
output reg[31:0] rdata2out,
output reg[31:0] s_extendout,
output reg[4:0] instrout_2016,
output reg[4:0] instrout_1511
);

```

```

initial begin

```

```

wb_ctlout <= 0;
    m_ctlout <= 0;
ex_ctlout <= 0;
    npcout <= 0;
    rdata1out <= 0;
    rdata2out <= 0;
    s_extendout <= 0;
    instrout_2016 <= 0;
    instrout_1511 <= 0;

```

```

end

```

```

always @*

```

```

begin

```

```

#1 // clock cycle of the latch

```

```

wb_ctlout <= ctlwb_out;
    m_ctlout <= ctlm_out;
    ex_ctlout <= ctlex_out;
    npcout <= npc;
    rdata1out <= readdat1;
    rdata2out <= readdat2;
    s_extendout <= signext_out;
    instrout_2016 <= instr_2016;
    instrout_1511 <= instr_1511;

```

```

end

```

```

endmodule

```

● The completed ID stage

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Engineer: Hau Tao
// Create Date: 16:23:46 11/12/2015
// Module Name:      final_ID_stage
/////////////////////////////////////////////////////////////////
module final_ID_stage(input[31:26] IR_control, input[31:0] npc_in, input[25:21] IR_reg1,
input[20:16] IR_reg2, input[15:0] unextended_bit,
    input[20:16] IR_mux0, input[15:11] IR_mux1, input WB, input[31:0]
mux_output_MEM_WB, input[4:0] MEM_WB,
    output wire [1:0] wb_ctlout,
    output wire [2:0] m_ctlout,
    output wire[3:0] ex_ctlout,
    output wire[31:0] npcout,
    output wire[31:0] rdata1out,
    output wire[31:0] rdata2out,
    output wire [31:0] s_extendout,
    output wire [4:0] instrout_2016,
    output wire [4:0] instrout_1511

);

wire [31:0] read_data_1;
wire [31:0] read_data_2;
wire [31:0] extended_signal_1;
wire [3:0] EX_out;
wire [2:0] MEM_out;
wire [1:0] WB_out;
register_file register1 (
    .reg_write(WB),
```

```

.rs(IR_reg1),
.rt(IR_reg2),
.rd(MEM_WB),
.write_data(mux_output_MEM_WB),
.A(read_data_1),
.B(read_data_2)
);

```

```

extended_register extended_register_1 (
    .unextended_signal(unextended_bit),
    .extended_signal(extended_signal_1)
);

```

```

control_bit control_bit_1(
    .opcode(IR_control),
    .EX(EX_out),
    .MEM(MEM_out),
    .WB(WB_out)
);

```

```

ID_latch ID_latch_1 (
    .ctlwb_out(WB_out),
    .ctlm_out(MEM_out),
    .ctlex_out(EX_out),
    .npc(npc_in),
    .readdat1(read_data_1),
    .readdat2(read_data_2),
    .signext_out(extended_signal_1),
    .instr_2016(IR_mux0),
    .instr_1511(IR_mux1),
    .wb_ctlout(wb_ctlout),
    .m_ctlout(m_ctlout),
    .ex_ctlout(ex_ctlout),
    .npcout(npcout),
    .rdata1out(rdata1out),
    .rdata2out(rdata2out),
    .s_extendout(s_extendout),
    .instrout_2016(instrout_2016),
    .instrout_1511(instrout_1511)
);

```

);

endmodule

- Connection IF_ID

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer: Hau Tao
```

```
//
```

```
// Create Date: 17:02:49 11/13/2015
```

```
// Design Name:
```

```
// Module Name: connectionID_IF
```

```
/
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module connectionID_IF(input PCSrc, input [31:0] EX_MEM,  
input WB,
```

```
    output wire [1:0] wb_ctlout,
```

```
    output wire [2:0] m_ctlout,
```

```
    output wire[3:0] ex_ctlout,
```

```
    output wire[31:0] npcout,
```

```
    output wire[31:0] rdata1out,
```

```
    output wire[31:0] rdata2out,
```

```
    output wire [31:0] s_extendout,
```

```
    output wire [4:0] instrout_2016,
```

```

        output wire [4:0] instrout_1511

    );
    wire [31:0] npcout_IF_ID;
    wire [31:0] instrout_IF_ID;

    IF_stage IF_1 (
        .PCSrc(PCSrc),
        .EX_MEM(EX_MEM),
        .npcout(npcout_IF_ID),
        .instrout(instrout_IF_ID)
    );

    // Instantiate the Unit Under Test (UUT)

    final_ID_stage uut (
        .IR_control(instrout_IF_ID[31:26]),
        .npc_in(npcout_IF_ID),
        .IR_reg1(instrout_IF_ID[25:21]),
        .IR_reg2(instrout_IF_ID[20:16]),
        .unextended_bit(instrout_IF_ID[15:0]),

```

```

.IR_mux0(instrout_IF_ID[20:16]),
.IR_mux1(instrout_IF_ID[15:11]),
.WB(WB),
.mux_output_MEM_WB(mux_output_MEM_WB),
.MEM_WB(MEM_WB),
.wb_ctlout(wb_ctlout),
.m_ctlout(m_ctlout),
.ex_ctlout(ex_ctlout),
.npcout(npcout),
.rdata1out(rdata1out),
.rdata2out(rdata2out),
.s_extendout(s_extendout),
.instrout_2016(instrout_2016),
.instrout_1511(instrout_1511)
);

```

```

always@*
# 20 $display("time =%0d\t instrout_IF_ID=%0b\t,
npcout_IF_ID=%0b\t", $time, instrout_IF_ID, npcout_IF_ID);

```

```

endmodule

```

E. Test bench design

1.The sign-extended unit

```
`timescale 1ns / 1ps
```

```
/////////////////////////////////////////////////////////////////
// Engineer: hau tao
// Create Date: 14:07:13 11/07/2015
// Design Name: extended_register
// Module Name:
/home/hau/Desktop/labcse401/lab2/ID_stage/test_extended_signal.v
// Project Name: ID_stage
/////////////////////////////////////////////////////////////////
```

```
module test_extended_signal;
```

```
    // Inputs
```

```
    reg [15:0] unextended_signal;
```

```
    // Outputs
```

```
    wire [31:0] extended_signal;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    extended_register uut (
        .unextended_signal(unextended_signal),
        .extended_signal(extended_signal)
    );
```

```
    initial begin
```

```
        // Initialize Inputs
```

```

unextended_signal = 0;

// Wait 1ns for global reset to finish

#1 unextended_signal = 16'b1110000100111111;
#2 unextended_signal = 16'b0000000100111111;
end
// Add stimulus here
always @*
begin
    #2 $display("Time = %0d\t unextended_signal =%0b\t
extended_signal=%0b\t", $time, unextended_signal, extended_signal);
    #1 $display("Time = %0d\t unextended_signal =%0b\t
extended_signal=%0b\t", $time, unextended_signal, extended_signal);
end
endmodule

```

2. The control unit

```
`timescale 1ns / 1ps

/////////////////////////////////////////////////////////////////
// Engineer: Hau Tao
//
// Create Date: 14:35:07 11/07/2015
// Design Name: control_bit
// Module Name: /home/hau/Desktop/labcse401/lab2/ID_stage/test_control_bit.v
// Project Name: ID_stage
/////////////////////////////////////////////////////////////////

module test_control_bit;

    // Inputs
    reg [5:0] opcode;

    // Outputs
    wire [3:0] EX;
    wire [2:0] MEM;
    wire [1:0] WB;

    // Instantiate the Unit Under Test (UUT)
    control_bit uut (
        .opcode(opcode),
        .EX(EX),
        .MEM(MEM),
        .WB(WB)
    );

    initial begin
        // Initialize Inputs
        opcode = 6'b000000;
        #2 opcode = 6'b100011;
        #4 opcode = 6'b101011;
        #6 opcode = 6'b000100;
```

end

always @*

begin

 #2 \$display("Time = %0d\t opcode = %0b\t EX = %0b\t MEM = %0b\t WB = %0b\t", \$time,
opcode, EX, MEM, WB);

 #4 \$display("Time = %0d\t opcode = %0b\t EX = %0b\t MEM = %0b\t WB = %0b\t", \$time,
opcode, EX, MEM, WB);

 #6 \$display("Time = %0d\t opcode = %1b\t EX = %0b\t MEM = %0b\t WB = %1b\t", \$time,
opcode, EX, MEM, WB);

end

endmodule

3. The register file

```
`timescale 1ns / 1ps

/////////////////////////////////////////////////////////////////
// Company:
// Engineer: hau tao
//
// Create Date: 15:34:02 11/07/2015
// Design Name: register_file
// Module Name: /home/hau/Desktop/labcse401/lab2/ID_stage/test_reg.v
// Project Name: ID_stage
/////////////////////////////////////////////////////////////////

module test_reg;

    // Inputs
    reg reg_write;
    reg [4:0] rs;
    reg [4:0] rt;
    reg [4:0] rd;
    reg [31:0] write_data;
    reg [31:0] register[0:4];

    integer i;

    // Outputs
    wire [31:0] A;
    wire [31:0] B;

    // Instantiate the Unit Under Test (UUT)
    register_file uut (
        .reg_write(reg_write),
        .rs(rs),
        .rt(rt),
        .rd(rd),
        .write_data(write_data),
        .A(A),
```



```

        .B(B)
    );

    initial begin
        // Initialize Inputs
        register[0] <= 'h002300AA;
        register[1] <= 'h10654321;
        register[2] <= 'h00100022;

        // 2ns delay
        #2
        begin
            reg_write = 1;
            rs = 1;
            rt = 2;
            rd = 2;
            write_data = 5;
        end

    end

    always@*
    begin
        #3 $display("Time = %0d\t rs =%0h\t rt=%0h\t rd=%0h\t write_data=%0h\t register[rd]
        =%0h\t A=%0h\t B=%1h\t", $time, rs, rt, rd, write_data,register[rd], A, B);

    end

endmodule

```

4. The ID/EX latch

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Engineer:Hau Tao
```

```
//
```

```
// Create Date: 15:49:27 11/12/2015
```

```
// Design Name: ID_latch
```

```
// Module Name: /home/hau/Desktop/labscse401/lab2/ID_stage/test_ID.v
```

```
////////////////////////////////////////////////////////////////
```

```
module test_ID;
```

```
    // Inputs
```

```
    reg [1:0] ctlwb_out;
```

```
    reg [2:0] ctlm_out;
```

```
    reg [3:0] ctlex_out;
```

```
    reg [31:0] npc;
```

```
    reg [31:0] readdat1;
```

```
    reg [31:0] readdat2;
```

```
    reg [31:0] signext_out;
```

```
    reg [4:0] instr_2016;
```

```
    reg [4:0] instr_1511;
```

```
    // Outputs
```

```
    wire [1:0] wb_ctlout;
```

```
    wire [2:0] m_ctlout;
```

```
    wire [3:0] ex_ctlout;
```

```
    wire [31:0] npcout;
```

```
    wire [31:0] rdata1out;
```

```
    wire [31:0] rdata2out;
```

```
    wire [31:0] s_extendout;
```

```
    wire [4:0] instrout_2016;
```

```
    wire [4:0] instrout_1511;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    ID_latch uut (
```

```

        .ctlwb_out(ctlwb_out),
        .ctlm_out(ctlm_out),
        .ctlex_out(ctlex_out),
        .npc(npc),
        .readdat1(readdat1),
        .readdat2(readdat2),
        .signext_out(signext_out),
        .instr_2016(instr_2016),
        .instr_1511(instr_1511),
        .wb_ctlout(wb_ctlout),
        .m_ctlout(m_ctlout),
        .ex_ctlout(ex_ctlout),
        .npcout(npcout),
        .rdata1out(rdata1out),
        .rdata2out(rdata2out),
        .s_extendout(s_extendout),
        .instrout_2016(instrout_2016),
        .instrout_1511(instrout_1511)
    );

```

initial begin

 // Initialize Inputs

 ctlwb_out = 0;

 ctlm_out = 0;

 ctlex_out = 0;

 npc = 0;

 readdat1 = 0;

 readdat2 = 0;

 signext_out = 0;

 instr_2016 = 0;

 instr_1511 = 0;

 // Wait 10 ns for global reset to finish

#10

 ctlwb_out = 1;

 ctlm_out = 2;

 ctlex_out = 3;

 npc = 4;

```
readdat1 = 5;  
readdat2 = 6;  
signext_out = 7;  
instr_2016 = 8;  
instr_1511 = 9;
```

```
//#10;  
//$finish;  
end
```

```
endmodule
```

5. The completed ID stage

```
`timescale 1ns / 1ps

/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 16:29:56 11/13/2015
// Design Name: final_ID_stage
// Module Name: /home/hau/Desktop/labcse401/lab2/ID_stage/testing_ID_stage.v
// Project Name: ID_stage
// Target Device:
// Tool versions:
// Description:
//
// Verilog Test Fixture created by ISE for module: final_ID_stage
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module testing_ID_stage;

    // Inputs
    reg [31:26] IR_control;
    reg [31:0] npc_in;
    reg [25:21] IR_reg1;
    reg [20:16] IR_reg2;
    reg [15:0] unextended_bit;
    reg [20:16] IR_mux0;
    reg [15:11] IR_mux1;
    reg WB;
    reg [31:0] mux_output_MEM_WB;
    reg [4:0] MEM_WB;
```

```

// Outputs
wire [1:0] wb_ctlout;
wire [2:0] m_ctlout;
wire [3:0] ex_ctlout;
wire [31:0] npcout;
wire [31:0] rdata1out;
wire [31:0] rdata2out;
wire [31:0] s_extendout;
wire [4:0] instrout_2016;
wire [4:0] instrout_1511;

// Instantiate the Unit Under Test (UUT)
final ID_stage uut (
    .IR_control(IR_control),
    .npc_in(npc_in),
    .IR_reg1(IR_reg1),
    .IR_reg2(IR_reg2),
    .unextended_bit(unextended_bit),
    .IR_mux0(IR_mux0),
    .IR_mux1(IR_mux1),
    .WB(WB),
    .mux_output_MEM_WB(mux_output_MEM_WB),
    .MEM_WB(MEM_WB),
    .wb_ctlout(wb_ctlout),
    .m_ctlout(m_ctlout),
    .ex_ctlout(ex_ctlout),
    .npcout(npcout),
    .rdata1out(rdata1out),
    .rdata2out(rdata2out),
    .s_extendout(s_extendout),
    .instrout_2016(instrout_2016),
    .instrout_1511(instrout_1511)
);

initial begin
    // Initialize Inputs
    IR_control = 0;
    npc_in = 0;

```

```
IR_reg1 = 0;
IR_reg2 = 0;
unextended_bit = 0;
IR_mux0 = 0;
IR_mux1 = 0;
WB = 0;
mux_output_MEM_WB = 0;
MEM_WB = 0;

// Wait 100 ns for global reset to finish
// Wait 100 ns for global reset to finish
#10
IR_control = 6'b000000;
npc_in = 2;
IR_reg1 = 0;
IR_reg2 = 2;
unextended_bit = 16'b1010111111101100;
IR_mux0 = 9;
IR_mux1 = 10;
WB = 1;
MEM_WB = 2;
mux_output_MEM_WB = 5;

// Add stimulus here
```

```
end
```

```
endmodule
```

6. Connection IF_ID

`timescale 1ns / 1ps

//

// Company:

// Engineer: Hau Tao

//

// Create Date: 17:37:38 11/13/2015

// Design Name: connectionID_IF

// Module Name: /home/hau/Desktop/labscse401/connection_ID_IF/testing_ID_IF.v

//

module testing_ID_IF;

// Inputs

reg PCSrc;

reg [31:0] EX_MEM;

reg WB;

// Outputs

wire [1:0] wb_ctlout;

wire [2:0] m_ctlout;

wire [3:0] ex_ctlout;

wire [31:0] npcout;

wire [31:0] rdata1out;

wire [31:0] rdata2out;

wire [31:0] s_extendout;

wire [4:0] instrout_2016;

wire [4:0] instrout_1511;

// Instantiate the Unit Under Test (UUT)

connectionID_IF uut (

.PCSrc(PCSrc),

.EX_MEM(EX_MEM),

.WB(WB),

.wb_ctlout(wb_ctlout),

.m_ctlout(m_ctlout),

.ex_ctlout(ex_ctlout),


```
.npcout(npcout),  
.rdata1out(rdata1out),  
.rdata2out(rdata2out),  
.s_extendout(s_extendout),  
.instrout_2016(instrout_2016),  
.instrout_1511(instrout_1511)  
);
```

```
initial begin
```

```
    // Initialize Inputs
```

```
    PCSrc = 0;
```

```
    EX_MEM = 0;
```

```
    WB = 0;
```

```
    // Wait 100 ns for global reset to finish
```

```
    #10;
```

```
    PCSrc = 1;
```

```
    EX_MEM = 1;
```

```
    WB = 1;
```


```
    // Add stimulus here
```

```
end
```

```
endmodule
```


E. Time Simulation

1. The sign-extended unit

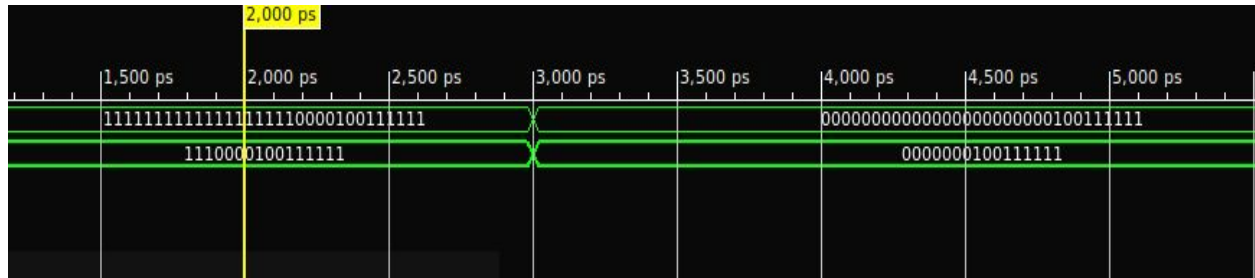

```
Time = 2  unextended_signal = 1110000100111111  extended_signal = 11111111111111111111000010011111
Time = 3  unextended_signal = 100111111  extended_signal = 11111111111111111111000010011111
```

2. The control unit

 

Time = 2	opcode =100011	EX=1100	MEM=000	WB=10
Time = 6	opcode =101011	EX=0001	MEM=010	WB=11
Time = 24	opcode =000100	EX=x010	MEM=100	WB=0x

3. The register file



4. The ID/EX latch

Name	Value	999,992 ps	999,993 ps	999,994 ps	999,995 ps	999,996 ps	999,997 ps
wb_ctlout[1:0]	01				01		
m_ctlout[2:0]	010				010		
ex_ctlout[3:0]	0011				0011		
npcout[31:0]	00000000000000000000000000000000			00000000000000000000000000000000	00000000000000000000000000000000		
rdata1out[31:0]	00000000000000000000000000000000			00000000000000000000000000000000	00000000000000000000000000000000		
rdata2out[31:0]	00000000000000000000000000000000			00000000000000000000000000000000	00000000000000000000000000000000		
s_extendout[31:0]	00000000000000000000000000000000			00000000000000000000000000000000	00000000000000000000000000000000		
instrout_2016[4:0]	01000				01000		
instrout_1511[4:0]	01001				01001		
ctlwb_out[1:0]	01				01		
ctlm_out[2:0]	010				010		
ctlex_out[3:0]	0011				0011		
npc[31:0]	00000000000000000000000000000000			00000000000000000000000000000000	00000000000000000000000000000000		
readdat1[31:0]	00000000000000000000000000000000			00000000000000000000000000000000	00000000000000000000000000000000		
readdat2[31:0]	00000000000000000000000000000000			00000000000000000000000000000000	00000000000000000000000000000000		
signext_out[31:0]	00000000000000000000000000000000			00000000000000000000000000000000	00000000000000000000000000000000		
instr_2016[4:0]	01000				01000		
instr_1511[4:0]	01001				01001		

Note: The first 9 variables are the values of output, the last 9 variables are values of input. It's apparent that the outputs are same exactly with the inputs. All values are hex represented

5. The completed ID/EX stage

Name	Value	999,992 ps	999,993 ps	999,994 ps	999,995 ps	999,996 ps
wb_ctlout[1:0]	2				2	
m_ctlout[2:0]	0				0	
ex_ctlout[3:0]	c				c	
npcout[31:0]	00000002				00000002	
rdata1out[31:0]	002300aa				002300aa	
rdata2out[31:0]	00000005				00000005	
s_extendout[31:0]	ffffafec				ffffafec	
instrout_2016[4:0]	09				09	
instrout_1511[4:0]	0a				0a	
IR_control[31:26]	00				00	
npc_in[31:0]	00000002				00000002	
IR_reg1[25:21]	00				00	
IR_reg2[20:16]	02				02	
unextended_bit[15:0]	afec				afec	
IR_mux0[20:16]	09				09	
IR_mux1[15:11]	0a				0a	
WB	1					
mux_output_MEM_WB[31:0]	00000005				00000005	
MEM_WB[4:0]	02				02	

Explanation: All values are hex representation

when IR_control opcode = 0x0, thw wb_ctlout = 0x2, m_ctlout = 0x0, ex_ctlout = 0xC

npc output = npc_in = 0x2

IR_mux0 = instrout_2016 = 0x9

IR_mux1 = instr_1511 = 0xA

unextended_bit = 0xafec => extended_bit = 0xffffafec

with WB= 1, it is enable register file and ready to read data from register file. rdata1out = 0x2300a which is reading content at register[0], and rdata2out = 0x10654321 which read from register[2]. at this time rd = 2, the content of register[rd] = register[2] = mux_output_MEM_WB = 0x5. Therefore, rda2out = 0x5

G. Conclusion

The purpose of this project is to implement ID module. I completed it successfully and the test cases is good enough .The most difficult part of this module is to implement register file, but due to clear explanation from professor and TA, I could finish it